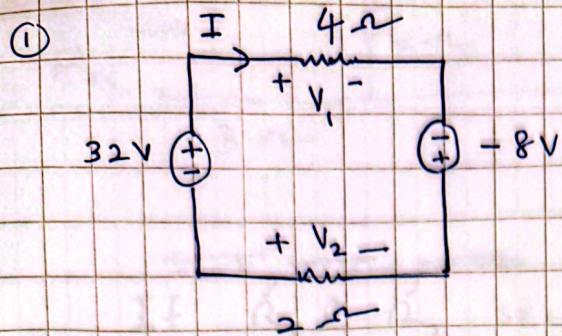


Analog Electronics - I Assignment 1. Madushan Rajapaksha.



Consider current I is flowing through the circuit.

$$\text{so } V_1 = I \times 4\Omega = 4I \rightarrow \textcircled{1}$$

$$V_2 = (-I) \times 2\Omega = -2I \rightarrow \textcircled{2}$$

Apply KVL (1)

$$-32V + V_1 - (-8V) - V_2 = 0$$

$$V_1 - V_2 = 24V \rightarrow \textcircled{3}$$

Substitute $\textcircled{1}$ & $\textcircled{2}$ to equation $\textcircled{3}$

$$4I - (-2I) = 24V$$

$$6I = 24V$$


$$\boxed{I = 4A}$$

So substitute $I = 4A$ to eq $\textcircled{1}$ & eq $\textcircled{2}$

$$V_1 = 4(+) = 16V \cancel{\quad}$$

$$V_2 = 4(-) = -8V \cancel{\quad}$$

(2)

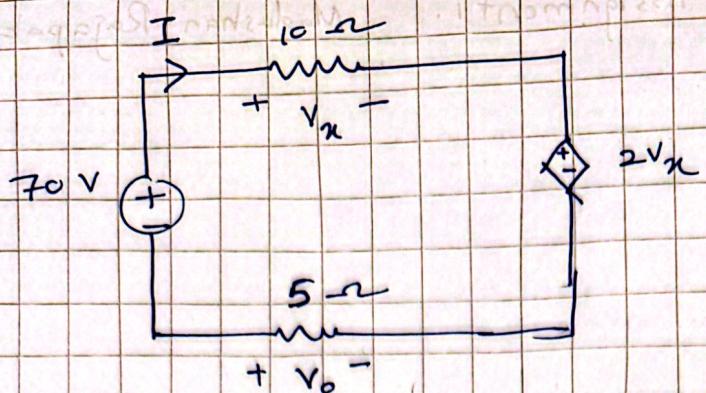

consider current I is flowing through the circuit.

$$\text{so } V_x = 10I$$

$$V_o = -5I$$

Apply KVL $\uparrow \Rightarrow$

$$-70 + V_x + 2V_x - V_o = 0$$

$$3V_x - V_o = 70$$

$$3(10I) - (-5I) = 70$$

$$35I = 70$$

$$\boxed{I = 2 \text{ A}}$$

$$\text{so } V_x = 10I$$


$$= 10(2)$$

$$\boxed{V_x = 20 \text{ V}}$$

$$V_o = 5I$$

$$= 5(2)$$

$$\boxed{V_o = 10 \text{ V}}$$

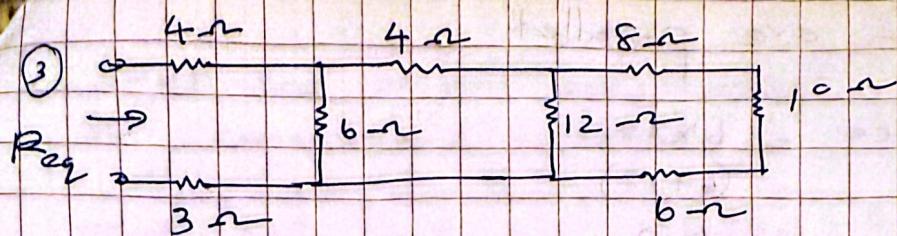


~~8 ohm, 10 ohm, 6 ohm in series~~
If R_1, R_2, R_3 series $R_{eq} = R_1 + R_2 + R_3$

If $R_1 \& R_2$ Parallel $R_{eq} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


So 8 ohm, 10 ohm, 6 ohm in series
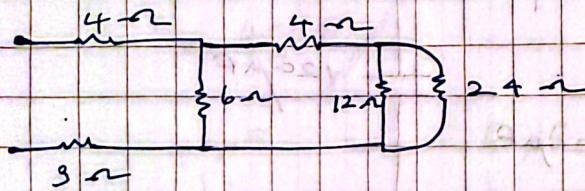
$$\text{So Resistance} = 8 + 10 + 6 \\ = 24 \text{ ohm}$$




12 ohm & 24 ohm parallel
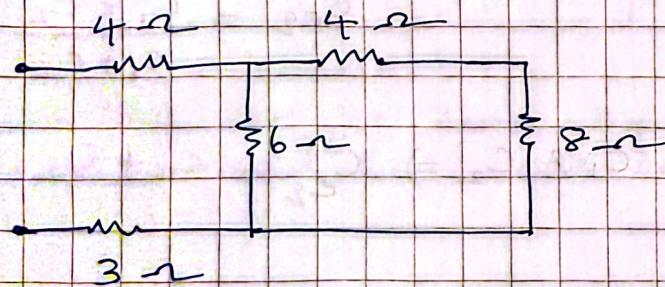
$$\text{So Resistance} = \frac{24 \times 12}{(24 + 12)} \\ = 8 \text{ ohm}$$




8 ohm 8 ohm 4 ohm series
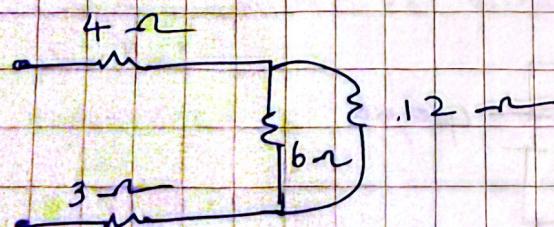
$$\text{So Resistance} = 8 \text{ ohm} + 4 \text{ ohm} \\ = 12 \text{ ohm}$$




6 Ω & 12 Ω are parallel
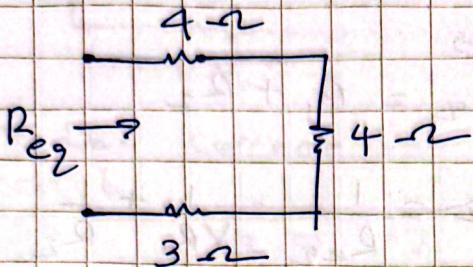
$$\text{So Resistance} = \frac{6 \times 12}{(6+12)} \\ = 4 \Omega$$


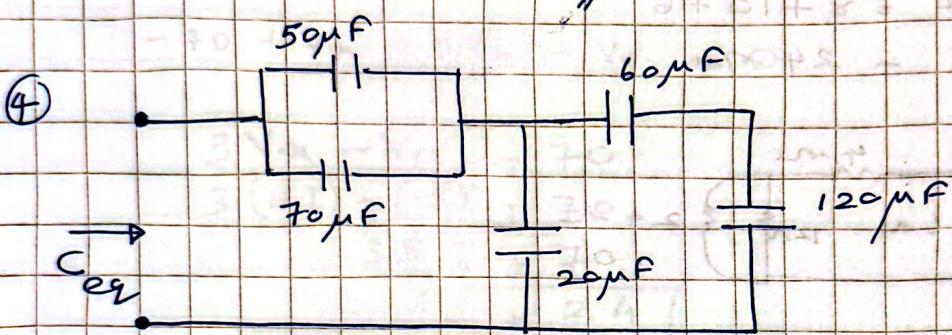
$$\text{So } R_{eq} = 4 \Omega + 4 \Omega + 3 \Omega \\ = 11 \Omega$$




$$\text{Series Capacitors } C_1 \text{ & } C_2 \Rightarrow C_{eq} = \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 \times C_2}{C_1 + C_2}$$

$$\text{Parallel Capacitors } C_1 \text{ & } C_2 \Rightarrow C_{eq} = C_1 + C_2$$


60 μF & 120 μF in series
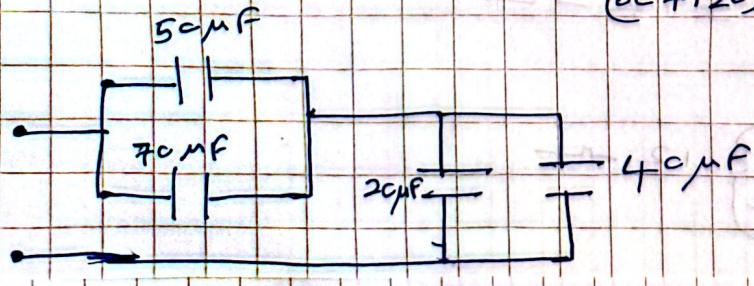
$$\text{So capacitance} = \frac{60 \times 120}{(60+120)} = 40 \mu\text{F}$$



$50\mu F$ and $70\mu F$ are parallel
so capacitance = $120\mu F$

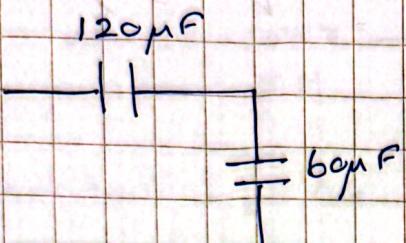
$20\mu F$ and $40\mu F$ are parallel
so capacitance = $20 + 40$
= $60\mu F$



$120\mu F$ and $60\mu F$ are series capacitors

$$\text{so } C_{eq} = \frac{120 \times 60}{(120+60)}$$

$$= 40\mu F$$

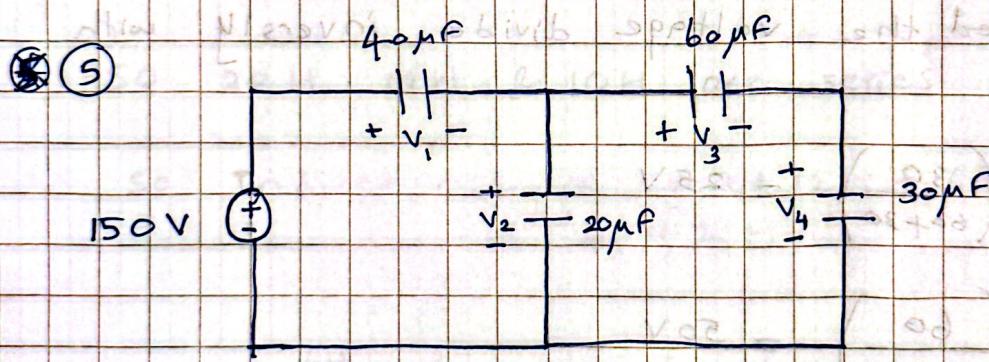

We can do this can be done by using voltage divider method. First need to simplify the circuit.


$60\mu F$ and $30\mu F$ are series. (V_3 & V_4 capacitors)

$$\text{so Capacitance} = \frac{60 \times 30}{90} = 20\mu F$$

This $20\mu F$ capacitor and V_2 voltage has $20\mu F$ capacitor. They are parallel.


$$\text{So capacitance of them} = 20\mu F + 20\mu F$$

$$= 40\mu F$$

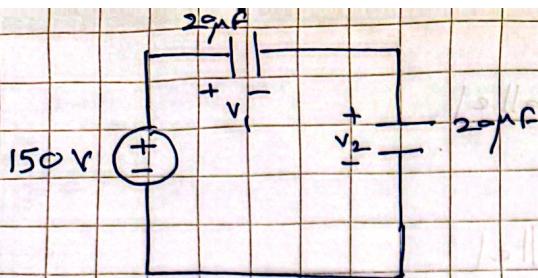

150 V divide in both V_1 & V_2 equally, because they have same capacitance.
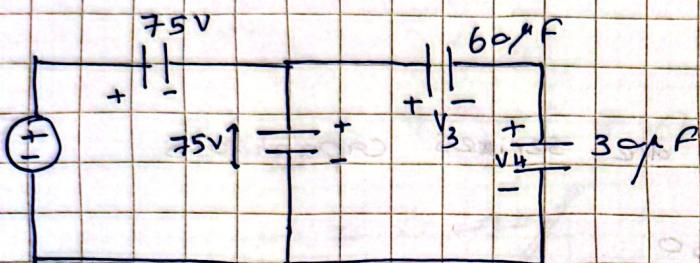
$$\text{So } V_1 = 75 \text{ V} \quad V_2 = 75 \text{ V}$$




This 75 V in V_2 is divide between $60\mu\text{F}$ and $30\mu\text{F}$. In capacitors smaller capacitance get more voltage.

So this method the voltage divide inversely with Capacitance.

$$V_3 = 75 \cdot \left(\frac{30}{60+30} \right) = 25 \text{ V}$$

$$V_4 = 75 \cdot \left(\frac{60}{60+30} \right) = 50 \text{ V}$$
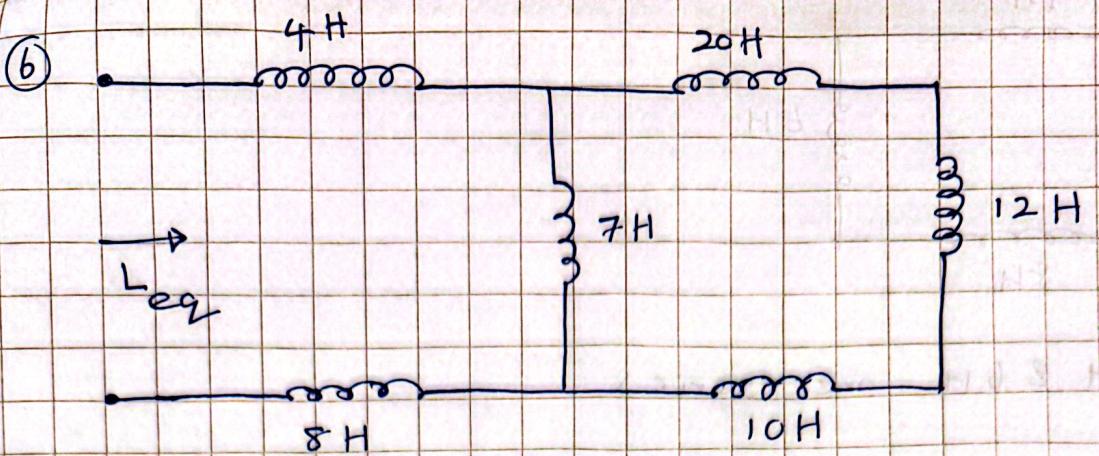
$$V_1 = 75 \text{ V} // V_2 = 75 \text{ V} // V_3 = 25 \text{ V} // V_4 = 50 \text{ V} //$$



If L_1 & L_2 are series inductors \Rightarrow

$$L_{eq} = L_1 + L_2$$


If L_1 and L_2 are parallel inductors \Rightarrow

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$


So 20H, 12H & 10H are series
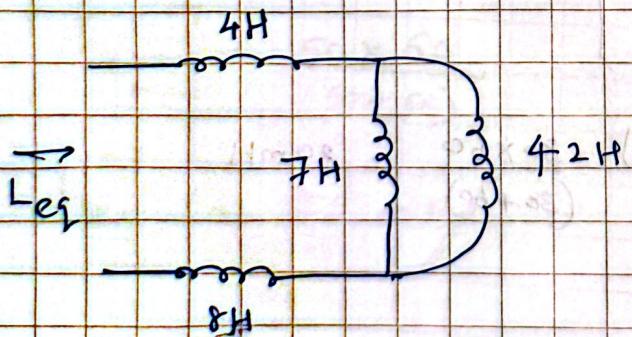
$$\begin{aligned} \text{So Inductance} &= 20H + 12H + 10H \\ &= 42H \end{aligned}$$



7H & 42H are parallel

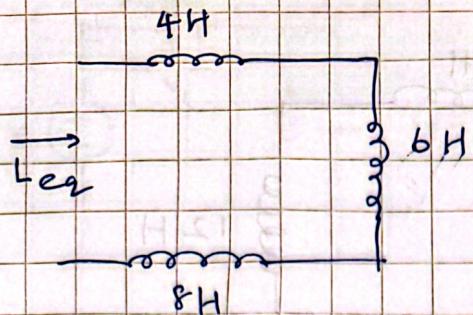
$$\text{So inductance} = \frac{42 \times 7}{42 + 7} = 6H$$



4H, 8H & 6H are series


$$\text{So } L_{\text{eq}} = 4\text{H} + 6\text{H} + 8\text{H}$$

$$L_{\text{eq}} = 18\text{H} //$$

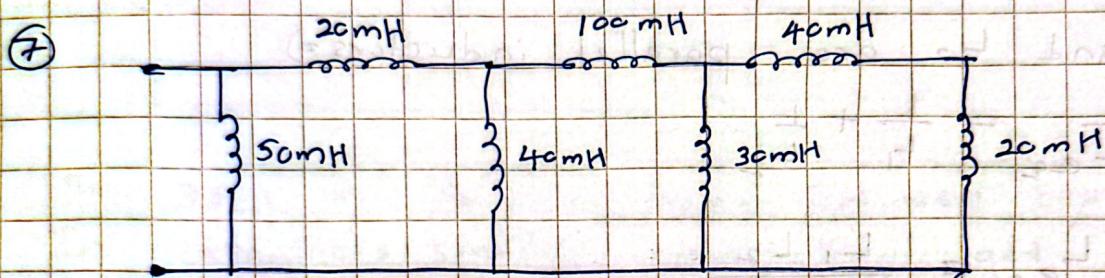


40mH & 20mH are series \Rightarrow

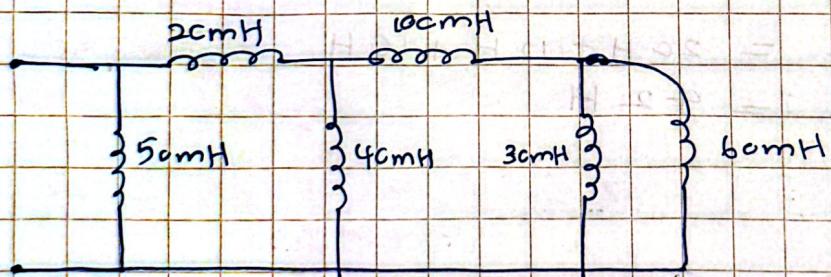
$$\text{So inductance} = 40 + 20 = 60\text{mH}$$



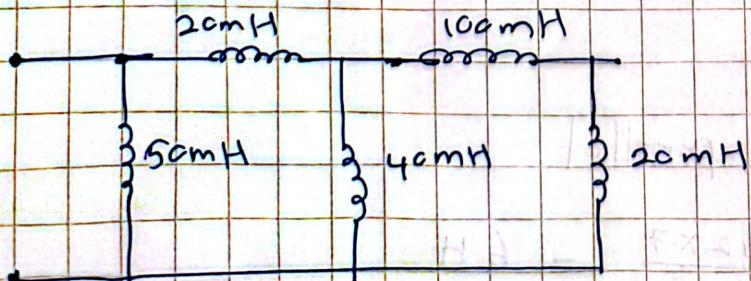
$$30\text{mH} \text{ & } 60\text{mH} \text{ parallel} \Rightarrow \frac{30 \times 60}{(30+60)} = 20\text{mH}$$



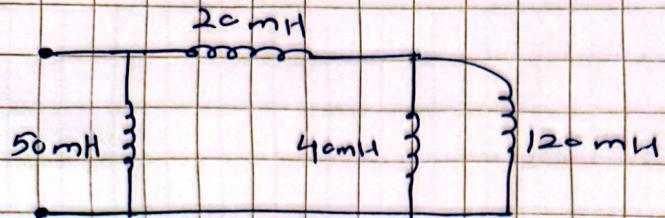
$$100 \text{ mH} \ \& \ 20 \text{ mH} \text{ series} \Rightarrow 100 \text{ mH} + 20 \text{ mH} \\ = 120 \text{ mH}$$


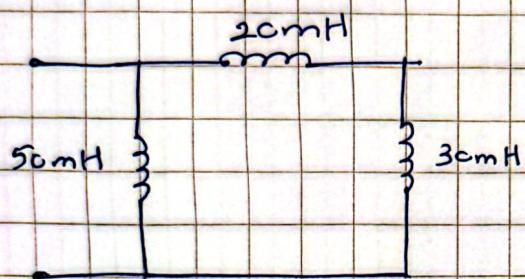
$$120 \text{ mH} \ \& \ 40 \text{ mH} \text{ parallel} \Rightarrow \frac{40 \times 120}{(40+120)} = 30 \text{ mH}$$


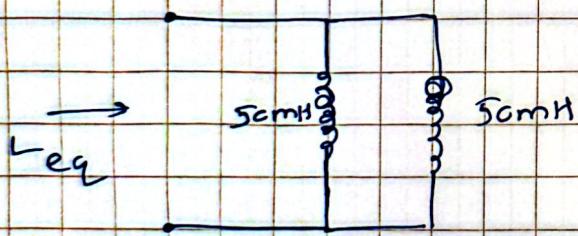
$$20 \text{ mH} \ \& \ 30 \text{ mH} \text{ series} \Rightarrow 30 \text{ mH} + 20 \text{ mH} = 50 \text{ mH}$$



$$50 \text{ mH} \ \& \ 50 \text{ mH} \text{ parallel}$$

$$L_{eq} = \frac{50 \times 50}{(50+50)}$$

$$L_{eq} = 25 \text{ mH} //$$