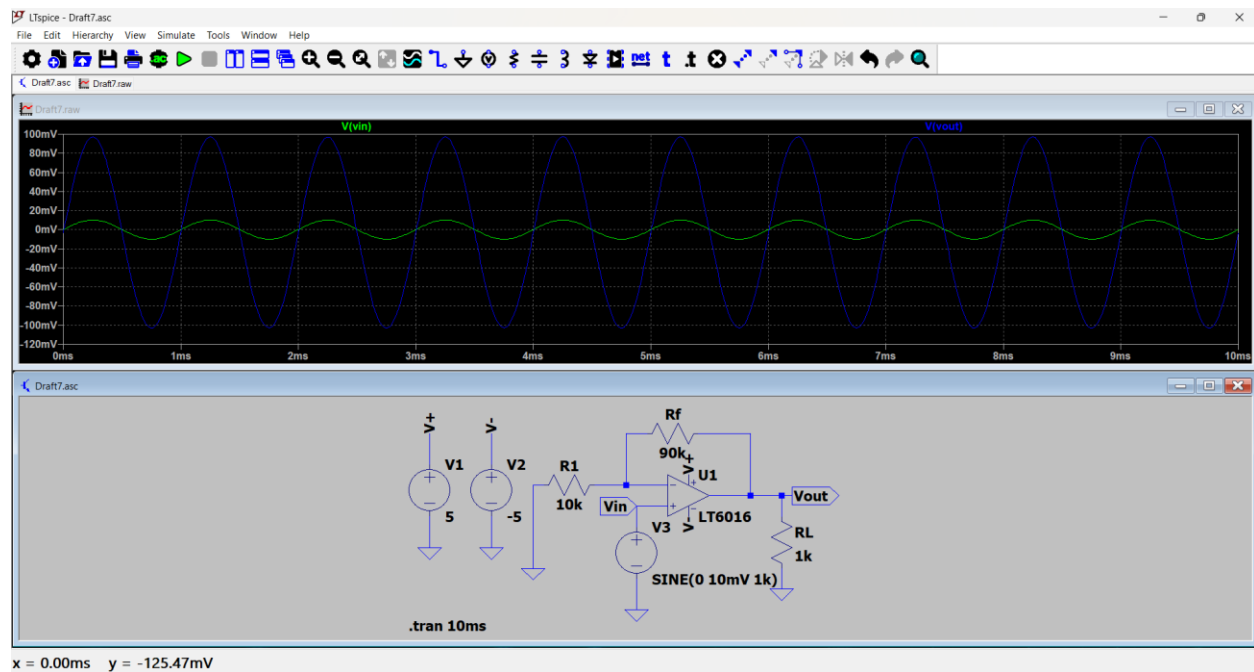




Task 2 – Non-Inverting Amplifier