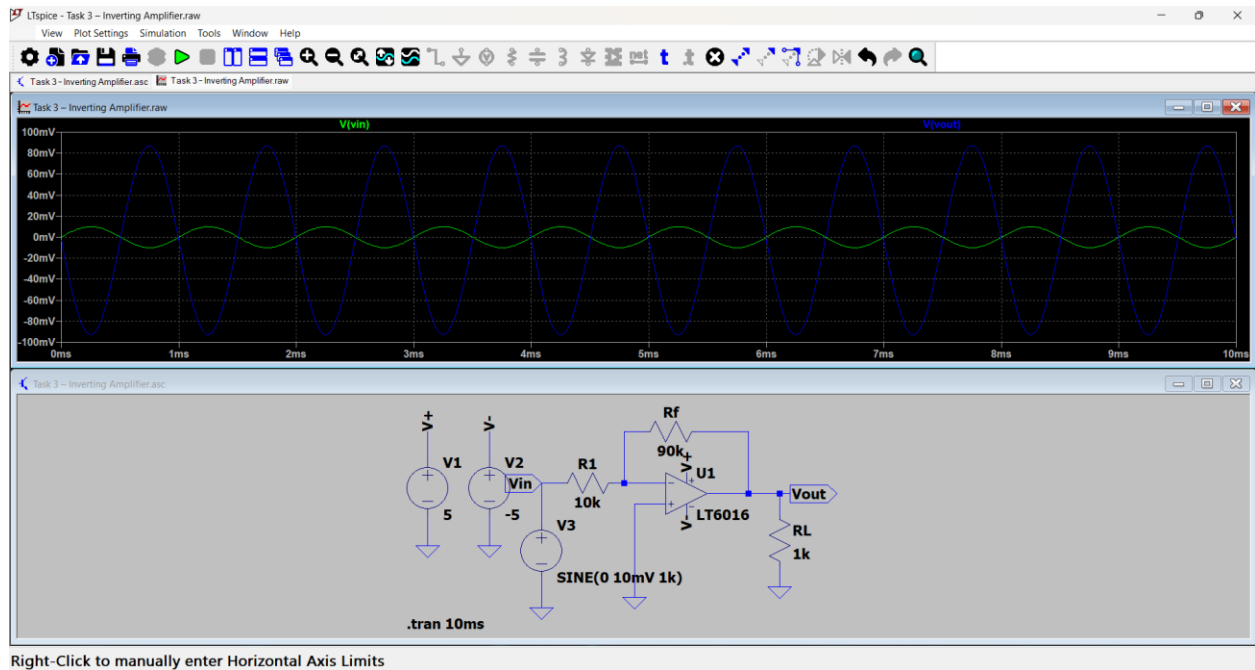




Task 3 – Inverting Amplifier